

## Control Unit Module Design – Structural Style Module Description

The control module design may be described in a **behavioral** or a **structural** style. The project can use modules described in both styles and both constructs can be used inside the same module.

### 1. Behavioral Style (*not entirely synthesizable, simulation*)

Example:

```
always@(opcode)
begin
    if (opcode == 4'b0011) //Store
    begin
        regWrite = 0;
        memtoReg = 0;
        PCtoReg = 0;
        branchN = 0;
        branchZ = 0;
        jump = 0;
        jumpMem=0;
        memRead = 0;
        memWrite = 1;
        aluOp = 4'b0100;
    end
end
end
```

### 2. Structural Style (*synthesizable, hardware implementation*)

The following module design is based on the DMUX and gates implementation (Figure 1) of the truth table presented in Figure 2 (partially).

```
#####
```

```
module control_clc(opcode, regWrite, memtoReg, PCtoReg, branchN, branchZ, jump, jumpMem, ALU,
memRead, memWrite);
```

```

input [3:0] opcode;

output [3:0] ALU;

output regWrite, memtoReg, PCtoReg, branchN, branchZ, jump, jumpMem, memRead, memWrite;

wire nS0, nS1, nS2, nS3;

wire [15:0] OUT;


integer E=1;

always@(opcode) begin
    if(opcode[0]==1'bZ) E=0;
end


DMUX_1_16 dmux_instance(E, opcode, OUT);

CLC_FUNCTIONS clc_functions_instance(.out(OUT), .rW(regWrite), .m2r(memtoReg), .pc2r(PCtoReg),
.bN(branchN), .bZ(branchZ), .jmp(jump), .jmpM(jumpMem), .alu(ALU), .memR(memRead),
.memW(memWrite));

endmodule

#####

module DMUX_1_16(E, opcode, out);

input wire E;

input [3:0] opcode;

output [15:0] out;

assign S[0] = opcode[0];

assign S[1] = opcode[1];

assign S[2] = opcode[2];

assign S[3] = opcode[3];


wire [3:0] S;

wire nS0, nS1, nS2, nS3;

```

```
//DMUX 1:16 Selectors
```

```
not(nS0, S[0]);
```

```
not(nS1, S[1]);
```

```
not(nS2, S[2]);
```

```
not(nS3, S[3]);
```

```
//DMUX 1:16 Outputs
```

```
nand(out[0], nS3, nS2, nS1, nS0, E);
```

```
nand(out[1], nS3, nS2, nS1, S[0], E);
```

```
nand(out[2], nS3, nS2, S[1], nS0, E);
```

```
nand(out[3], nS3, nS2, S[1], S[0], E);
```

```
nand(out[4], nS3, S[2], nS1, nS0, E);
```

```
nand(out[5], nS3, S[2], nS1, S[0], E);
```

```
nand(out[6], nS3, S[2], S[1], nS0, E);
```

```
nand(out[7], nS3, S[2], S[1], S[0], E);
```

```
nand(out[8], S[3], nS2, nS1, nS0, E);
```

```
nand(out[9], S[3], nS2, nS1, S[0], E);
```

```
nand(out[10], S[3], nS2, S[1], nS0, E);
```

```
nand(out[11], S[3], nS2, S[1], S[0], E);
```

```
nand(out[12], S[3], S[2], nS1, nS0, E);
```

```
nand(out[13], S[3], S[2], nS1, S[0], E);
```

```
nand(out[14], S[3], S[2], S[1], nS0, E);
```

```
nand(out[15], S[3], S[2], S[1], S[0], E);
```

```
endmodule
```

```
#####
```

```
module CLC_FUNCTIONS(out, alu, rW, m2r, pc2r, bN, bZ, jmp, jmpM, memR, memW);
```

```
input [15:0] out;
```

```
output rW, m2r, pc2r, bN, bZ, jmp, jmpM, memR, memW;
```

```
output [3:0] alu;
```

```
nand(rW, out[4], out[5], out[6], out[7], out[14], out[15]);
```

```
not(m2r, out[14]);
```

```
not(pc2r, out[15]);
```

```
not(bN, out[11]);
```

```
not(bZ, out[9]);
```

```
not(jmp, out[8]);
```

```
not(jmpM, out[10]);
```

```
nand(memR, out[10], out[14]);
```

```
not(memW, out[3]);
```

```
//ALU control unit, selectors
```

```
nand(alu[3], out[1], out[2]);
```

```
nand(alu[2], out[0], out[3], out[8], out[9], out[10], out[11], out[14], out[15]);
```

```
nand(alu[1], out[6], out[7]);
```

```
nand(alu[0], out[5], out[7]);
```

```
endmodule
```

```
#####
```

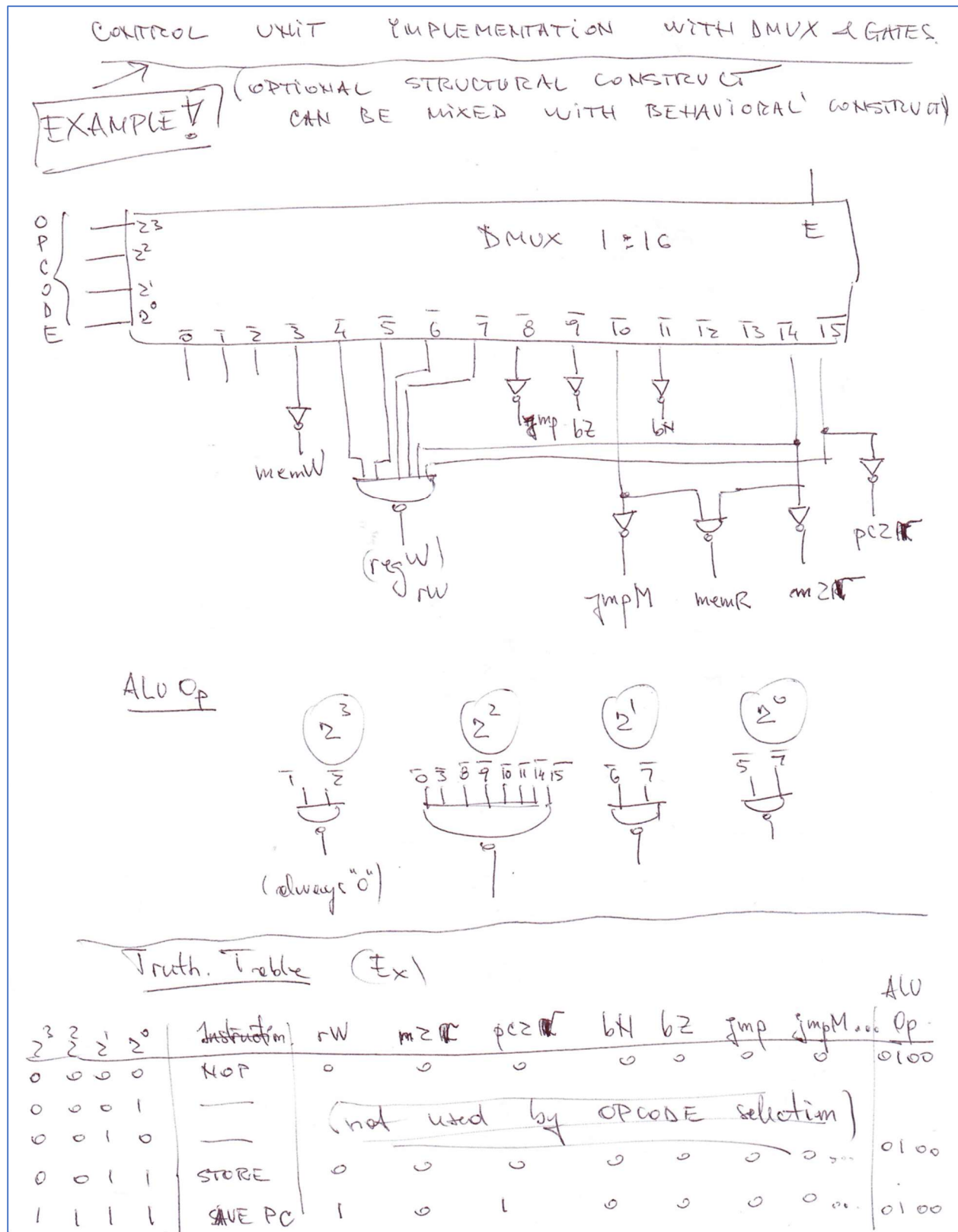


Figure 1: CLC Implementation of the Control Unit (Figure 2 Truth Table, with DMUX & Gates)

Instr uction	Op- code	regW rite	mem toRe g	PCto Reg	bran chN	bran chZ	jump	jump Mem	mem Read	mem Writ e	aluO p
NOP	0000	0									0100
Save PC	1111	1									0100
Load	1110	1									0100
Store	0011	0	0	0	0	0	0	0	0	1	0100
Add	0100	1	0	0	0	0	0	0	0	0	0000
Incre ment	0101	1									0001
Nega te	0110	1									0010
Subtr act	0111	1									0011
Jump	1000	0									0100
Bran ch if Z	1001	0									0100
Jump Mem	1010	0									0100
Bran ch if N	1011	0									0100

Figure 2: Truth Table Example