



# Arithmetic Logic Unit

COEN 122 Lab 2



# Grading

---

- Lab 1-4 (10% each) 40%
- Final Project 60%



# Late Policy

---

- Late submissions submitted within 24 hours after the deadline receive 50% credit. After 24 hours, no credit is given.



# Demo

---

- Labs submitted with no demo will receive no credit. Please demo to me before the lab is due.
- You can demo in either TAs Office Hours



# Lab 2 Overview

- Objective: Implement a 32-bit ALU in Verilog using Vivado with a gate level implementation
- For the first 4 labs, you will be working individually, but will be working in teams for the project

Helpful website: <http://www.asic-world.com/verilog/veritut.html>



# Design Flow

- Write code for logic block (e.g. 1-bit adder, full adder, 2-1 mux, 3-1 mux, 2s complement generator, selector)
- Write test bench to verify proper function of logic block
- Run Synthesis
- Run Simulation
- View waveform, verify results




# 6 Modules to Build

---

- ALU
- 2:1 Mux
- 3:1 Mux
- 2's Complement Generator
- 1 Bit Adder
- Full Adder




## 2:1 Mux Circuit Diagram

 






# 3:1 Mux Circuit Diagram

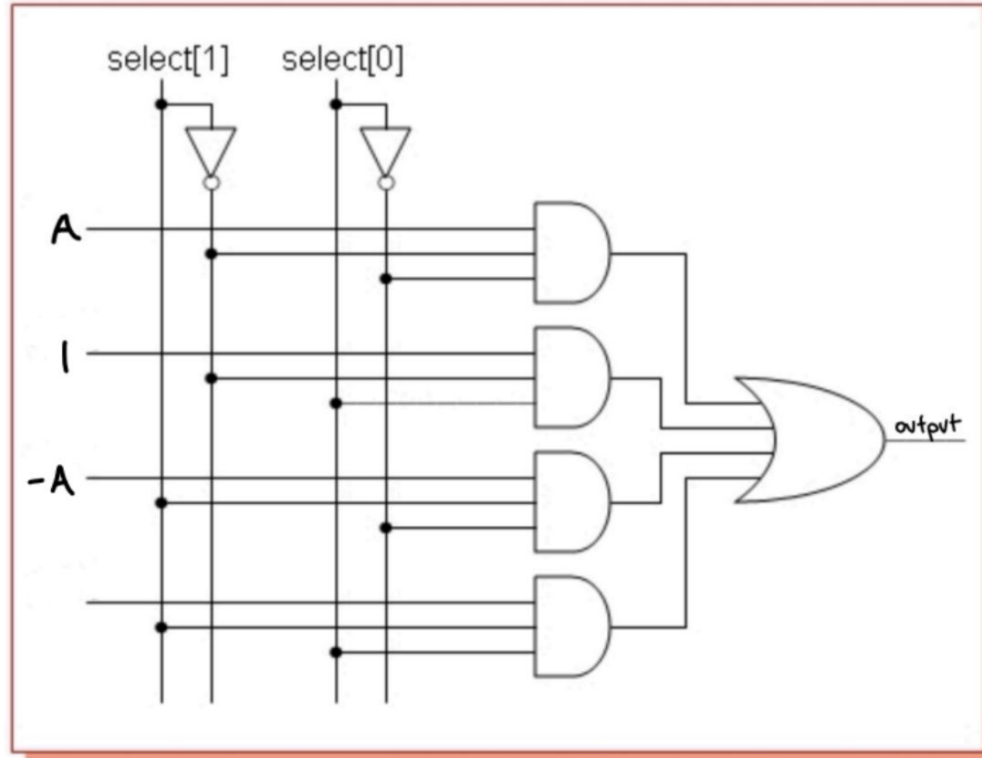




# 1 Bit Adder Circuit Diagram

 



 
## Ripple Carry Full Adder Circuit Diagram





# ALU Diagram

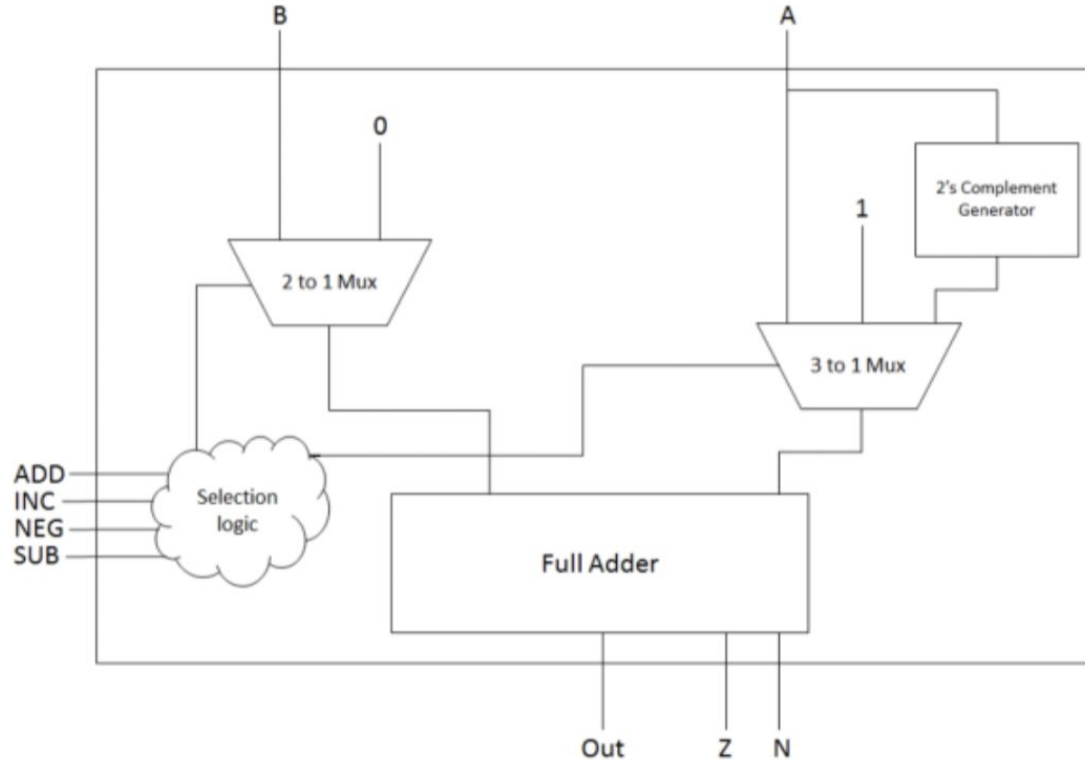



# Generating Selects for Each Mux

- For 3:1 Mux:
  - `not(not_sub, sub);`
  - `and(select[0], inc, not_sub);`
  - `nor(select[1], add, inc);`
- For 2:1 Mux:
  - `twoToOne mux_B(B, neg, outB), where select = neg`



# Module Definitions

- `module ALU(A,B,add,inc,neg,sub,out,Z,N);`
- `module twoToOne(B,sel,out);`
- `module oneBitAdder(A, B, cin, cout, out);`
- `module fullAdder(A, B, cout, sum);`
- `module negate(A, out);`
- `module threeToOne(A, negA, sel, out);`



# ALU Truth Table

ADD	INC	NEG	SUB	OUT	Operation
1	0	0	0	$B + A$	Add
0	1	0	0	$B + 1$	Increment
0	0	1	0	$-A$	2's complement
0	0	0	1	$B - A$	Subtract
1	1	1	1	A	Pass A



# Notes

- NEGATE operator should return 2's complement, so just flipping the bits won't be sufficient (need to add 1 to the resulting value)
- For SUBTRACT, remember to add the 2's complement of A
- Test Cases:
  - Add
  - Increment
  - Negate
  - Subtract
  - Pass





# Submission

---

- All ALU files as txt files
- ALU\_testbench file as a txt file
- Screenshot of waveform